

LINEAR NETWORKS ANALYSIS AND SYNTHESIS

LAB 1 SESSION 1 - SSS ANALYSIS OF A Sallen-Key Circuit

ACADEMIC YEAR 2023-2024

ALONSO HERREROS COPETE
NIA: 100493990

PREPARATORY HOMEWORK

The circuit in the figure 2 shows a well-known and widely used circuit often referred to as *Sallen-Key*


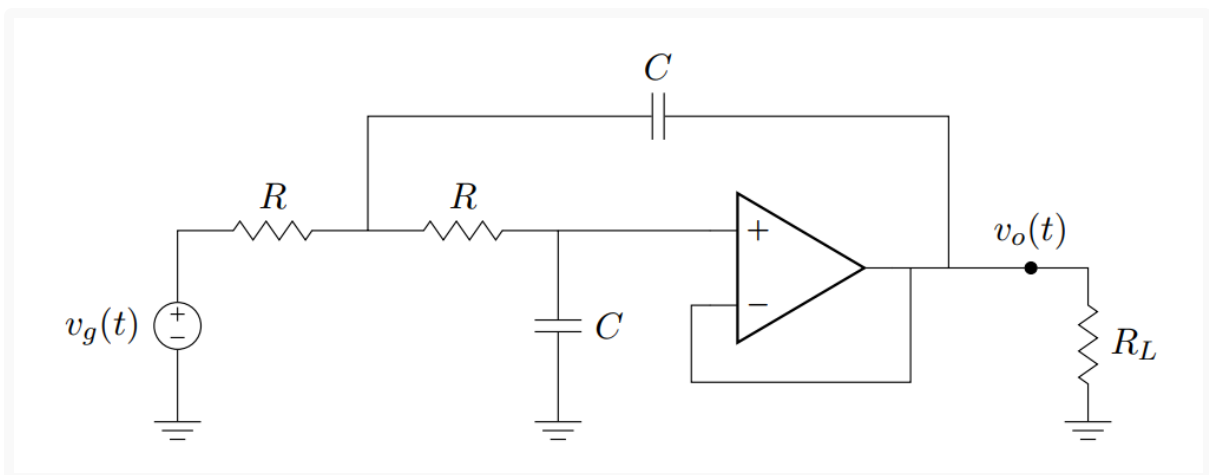


Figure 2: Sallen-Key Circuit

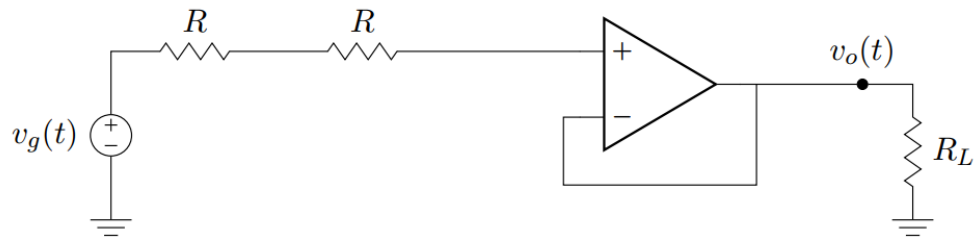1. In view of the circuit, estimate without calculating the transfer function the value of $V_o(\omega)/V_g(\omega)$ for $\omega = 0$ and $\omega = \infty$. Recall that the impedance of a capacitor depends on the angular frequency ω of the signal.

We can use the fact that capacitors act as open circuits at $\omega = 0$ and as short circuits at $\omega = \infty$ to estimate the behavior of the circuit at these frequencies. The Operational Amplifier is in a *voltage buffer* (also known as *voltage follower*) configuration, which has a gain of 1.

At $\omega = 0$, both capacitors act as **open circuits**, resulting in the following equivalent circuit:




Having an ideal OpAmp, the currents at both input terminals are zero.

$$i_+ = i_- = 0 \implies v_+ = v_g$$

From the voltage follower behavior, we can conclude that $v_o(t) = v_g(t)$ when $\omega = 0$, so the transfer function is $V_o(\omega)/V_g(\omega) = 1$ at $\omega = 0$.

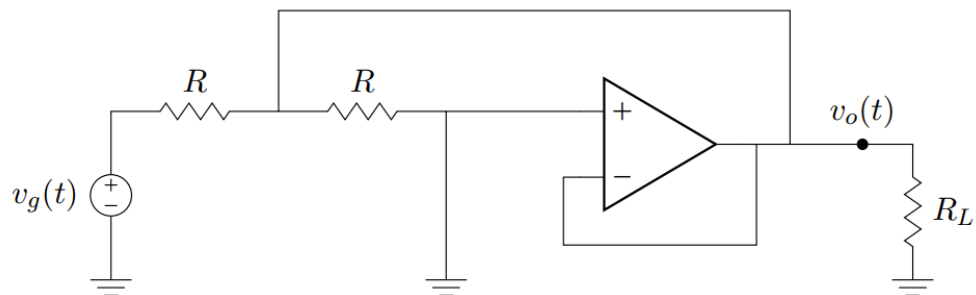At $\omega = \infty$, both capacitors act as **short circuits**, resulting in the following equivalent circuit.



Due to the shorting to ground at the positive OpAmp terminal, the input to the *voltage buffer* will always be 0.


$$v_+ = 0 \implies v_o = 0$$

This might seem contradicting with the same output node being connected to the point between both R resistors, but it's actually compatible: the voltage at this point is also 0, and no current flows through the second R resistor. All current going through the first R resistor is drained through the input of the ideal Operational Amplifier, which has 0 output impedance, keeping the voltage at v_o equal to 0. Therefore, the transfer function is $V_o(\omega)/V_g(\omega) = 0$ at $\omega = \infty$.

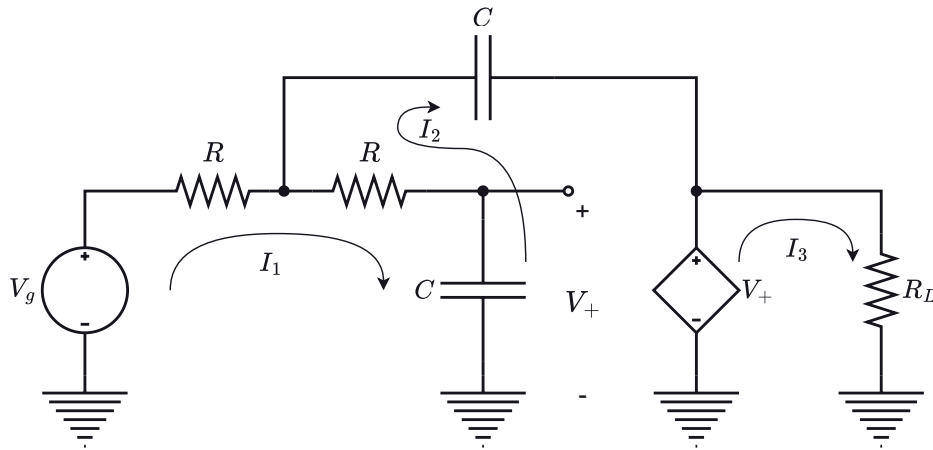2. Assume that the circuit works in sinusoidal steady state and obtain the transfer function defined by the following ratio:

$$H(\omega) = \frac{V_o(\omega)}{V_g(\omega)}$$

Using the following [equivalent circuit](#), we can perform mesh analysis and come up with three mesh equations to solve for the currents I_1 , I_2 and I_3 .



$$\begin{aligned} V_g &= I_1 \left(2R + \frac{1}{j\omega C} \right) - I_2 \left(R + \frac{1}{j\omega C} \right) \\ 0 &= -I_1 \left(R + \frac{1}{j\omega C} \right) + I_2 \left(R + \frac{2}{j\omega C} \right) + V_+ \\ V_+ &= I_3 (R_L) \end{aligned}$$

Using the substitution $V_+ = (I_1 - I_2) \frac{1}{j\omega C}$, we can rewrite the equations as:

$$\begin{aligned} V_g &= I_1 \left(2R + \frac{1}{j\omega C} \right) - I_2 \left(R + \frac{1}{j\omega C} \right) \\ 0 &= -I_1 (R) + I_2 \left(R + \frac{1}{j\omega C} \right) \\ 0 &= -I_1 \frac{1}{j\omega C} + I_2 \frac{1}{j\omega C} + I_3 (R_L) \end{aligned}$$

This can then be expressed in matrix form:

$$\begin{bmatrix} 2R + \frac{1}{j\omega C} & -R - \frac{1}{j\omega C} & 0 \\ -R & R + \frac{1}{j\omega C} & 0 \\ \frac{-1}{j\omega C} & \frac{1}{j\omega C} & R_L \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

We can solve it using Cramer's rule:

$$\begin{aligned} \det(A) &= \begin{vmatrix} 2R + \frac{1}{j\omega C} & -\left(R + \frac{1}{j\omega C}\right) & 0 \\ -R & R + \frac{1}{j\omega C} & 0 \\ \frac{-1}{j\omega C} & \frac{1}{j\omega C} & R_L \end{vmatrix} \\ &= R_L \left(\left(2R + \frac{1}{j\omega C} \right) \left(R + \frac{1}{j\omega C} \right) - R \left(R + \frac{1}{j\omega C} \right) \right) \\ &= R_L \left(R + \frac{1}{j\omega C} \right)^2 \end{aligned}$$

$$\begin{aligned}
 I_1 &= \frac{\begin{vmatrix} V_g & -R - \frac{1}{j\omega C} & 0 \\ 0 & R + \frac{1}{j\omega C} & 0 \\ 0 & \frac{1}{j\omega C} & R_L \end{vmatrix}}{\det(A)} = \frac{R_L V_g \left(R + \frac{1}{j\omega C} \right)}{R_L \left(R + \frac{1}{j\omega C} \right)^2} = \frac{1}{R + \frac{1}{j\omega C}} V_g \\
 I_2 &= \frac{\begin{vmatrix} 2R + \frac{1}{j\omega C} & V_g & 0 \\ -R & 0 & 0 \\ \frac{-1}{j\omega C} & 0 & R_L \end{vmatrix}}{\det(A)} = \frac{R_L V_g R}{R_L \left(R + \frac{1}{j\omega C} \right)^2} = \frac{R}{\left(R + \frac{1}{j\omega C} \right)^2} V_g \\
 I_3 &= \frac{\begin{vmatrix} 2R + \frac{1}{j\omega C} & -\left(R + \frac{1}{j\omega C} \right) & V_g \\ -R & R + \frac{1}{j\omega C} & 0 \\ \frac{-1}{j\omega C} & \frac{1}{j\omega C} & 0 \end{vmatrix}}{\det(A)} = \frac{V_g \left(-R + R + \frac{1}{j\omega C} \right) \frac{1}{j\omega C}}{R_L \left(R + \frac{1}{j\omega C} \right)^2} \\
 &= \frac{1}{R_L (j\omega CR + 1)^2} V_g
 \end{aligned}$$

Finally, we can use the current I_3 to obtain the output voltage, and divide by the input voltage to obtain the transfer function $H(\omega)$:

$$H(\omega) = \frac{V_o(\omega)}{V_g(\omega)} = \frac{I_3 R_L}{V_g} = \frac{1}{(j\omega CR + 1)^2}$$

3. Find the ratio between the square of the amplitudes of the input $v_g(t)$ and the output $v_o(t)$ for each angular frequency ω . That is:

$$|H(\omega)|^2 = \frac{|V_o(\omega)|^2}{|V_g(\omega)|^2}$$

This is a matter of squaring the magnitude of the transfer function obtained above. Using some properties of the magnitudes of products and quotients, it becomes a simple task:

$$\begin{aligned}
 |H(\omega)|^2 &= \frac{|V_o(\omega)|^2}{|V_g(\omega)|^2} \\
 &= \left| \frac{1}{(j\omega CR + 1)^2} \right|^2 \\
 &= \frac{|1|}{|j\omega CR + 1|^4} \\
 &= \frac{1}{(\sqrt{\omega^2 C^2 R^2 + 1})^4} \\
 &= \frac{1}{(\omega^2 C^2 R^2 + 1)^2}
 \end{aligned}$$

4. Determine, as a function of R and C , the angular frequency ω in which the amplitude of the output signal $v_o(t)$ is 3 dB lower than the amplitude of the input signal $v_g(t)$. That is, to find the angular frequency ω that verify

$$|H(\omega)|^2 = \frac{1}{2}$$

Using the previous result, we can obtain this by solving for ω in the resulting equation:

$$\begin{aligned} |H(\omega)|^2 = \frac{1}{2} &\iff \frac{1}{(\omega^2 C^2 R^2 + 1)^2} = \frac{1}{2} \implies \\ &\implies \omega^2 C^2 R^2 + 1 = \sqrt{2} \implies \\ &\implies \omega = \frac{\sqrt{\sqrt{2} - 1}}{CR} \end{aligned}$$

5. Calculate the current provided by the operational amplifier as a function of V_g , R , C , R_L and ω .

I will assume that the current *provided* by the Operational Amplifier refers only to the current that flows through the load resistor R_L , and not the the current coming from the top capacitor, which flows through the output terminal of the OpAmp.

This output current is the same as the current I_3 calculated above:

$$I_o(V_g, R, C, R_L, \omega) = I_3 = \frac{V_g}{R_L(j\omega CR + 1)^2}$$

6. The datasheet of the operational amplifier to be used specifies that the amplitude of the output current must always be less than 25 mA. If $R_L = 50\Omega$, what is the maximum value that the input signal amplitude can take in order not to exceed this margin when $\omega \approx 0$?

The previous consideration about the *output current* will be used. However, it's worth noting that the amplifier would sustain greater *input* currents at its *output* due to the currents from the capacitor mentioned above.

Due to the low frequency, we can simplify the equation for the output current I_o and easily calculate the maximum input signal amplitude V_g that to prevent exceeding the 25 mA output limit.

$$\begin{aligned} I_o &= \frac{V_g}{R_L \underbrace{(j\omega CR + 1)^2}_{\approx 0}} \approx \frac{V_g}{R_L} \\ |I_o| < I_{o;max} &\implies \left| \frac{V_g}{R_L} \right| < I_{o;max} \implies \\ &\implies |V_g| < R_L I_{o;max} = 50 \Omega \cdot 25 \text{ mA} = 1.25 \text{ V} \end{aligned}$$

The input voltage should not exceed $\pm 1.25 \text{ V}$ to comply with the output limits specified in the datasheet.

NOTE: It is recommended to check with the simulator the results obtained for a particular election of R and C

Falstad Circuit Link

The results were not completely consistent with the simulation, but the theoretical calculations, formulas and equations were checked against multiple sources.