

LINEAR NETWORKS ANALYSIS AND SYNTHESIS. LAB 1, APRIL 2024

SESSION 2

FULL NAME: Alonso Herreros Copete **DEGREE/GROUP:** Telecommunication Technologies Engineering / 95 **DATE and TIME:** Friday 12th April 2024, 11:00 **CLASSROOM:** Room 4.1.E05


1. MEASUREMENT OF THE VOLTAGE AND CURRENT AT THE OUTPUT OF THE MICROCONTROLLER

This [link](#) shows the simulation of a circuit where the relay that you have studied in the preparatory work is used to activate/deactivate a led. From this circuit diagram:

- Add an ammeter to measure the current flowing through the relay coil when the switch is activated. Comment what the ideal impedance of an ammeter would be taking into account that its objective is to measure current without disturbing the circuit.
- Add a voltmeter to measure the voltage at the output pin of the microcontroller (the connector one on the right of the switch, voltage $v_o(t)$ in the preparatory work). Comment what would be the ideal impedance of a voltmeter considering that its purpose is to measure voltage without disturbing the circuit.

The ideal impedance of the ammeter would be zero, acting as a simple wire that reports the current flowing through it.

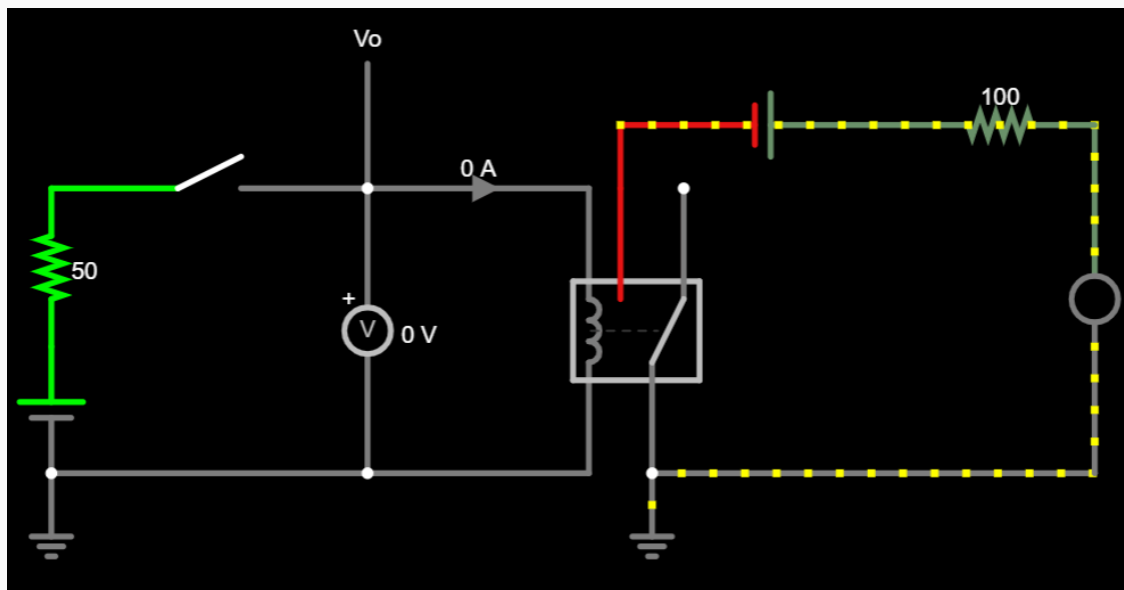The ideal impedance of the voltmeter would be infinite, acting as an open circuit "connected" to ground (the reference point) and measuring the voltage at the point where it is connected.




Falstad Link: <https://tinyurl.com/29rojfxa>

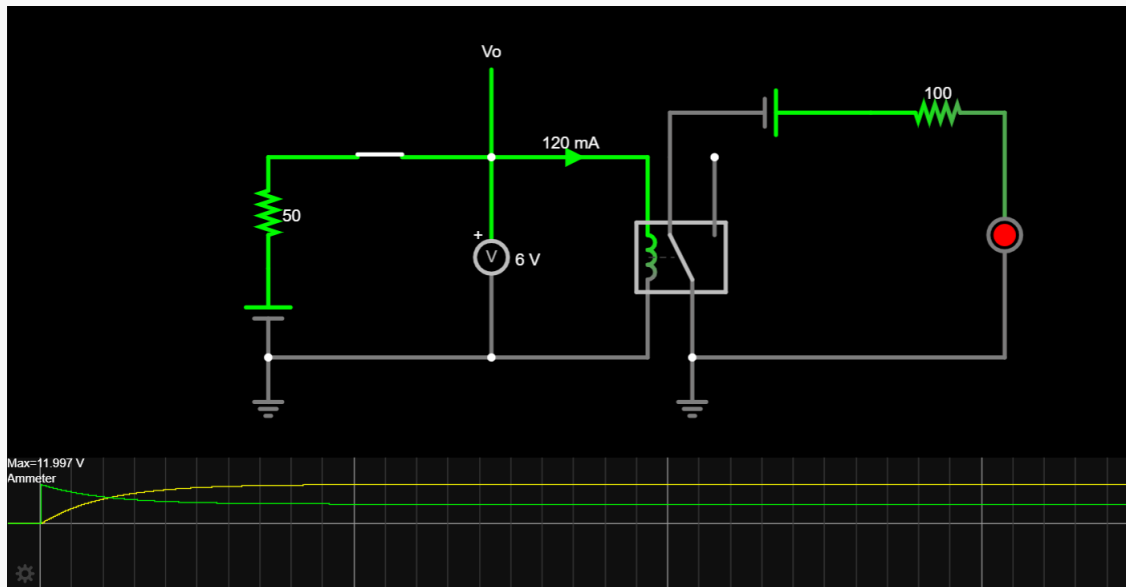2. STATIONARY CURRENT OF THE RELAY ACTIVATED

When the relay is activated, what value does the current flowing through the relay coil tend to after a long time? Relate the result with what was seen in the preparatory work. [2%]

After a long time, the current tends to 120 mA, as seen in the preparatory work. Although it is not shown in the circuit diagram, the relay is modeled as a coil with a 1 H inductance and 50 Ω resistance, just as the one studied in the preparatory work.




Falstad Link: <https://tinyurl.com/249rqayr>

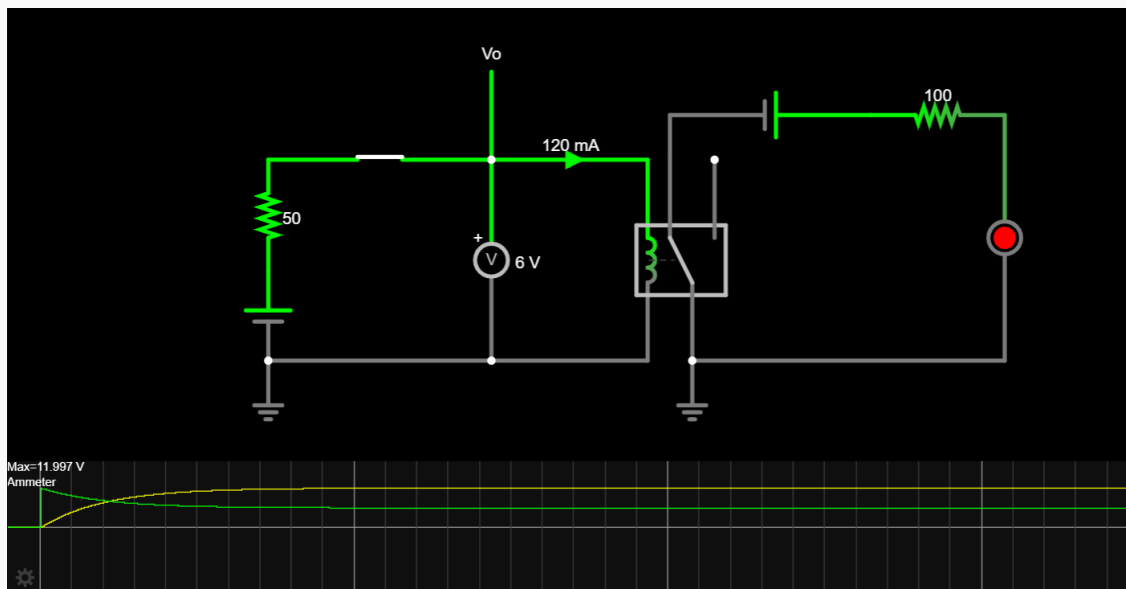3. STATIONARY VOLTAGE AT THE OUTPUT OF THE MICROCONTROLLER

When the relay is activated, to what value does the voltage at the output pin $v_o(t)$? Justify theoretically the result obtained.

The voltage at the output pin $v_o(t)$ tends to 6 V, as expected from the previous work. This is because, after a long time, the relay's inductor behaves as a short circuit, the two remaining resistors act as a voltage divider, with the measured voltage at the output pin being in the middle of both 50 Ω resistors. As a result, the generator voltage of 12 V is divided in half, giving us 6 V.




Falstad Link: <https://tinyurl.com/249rqayr>

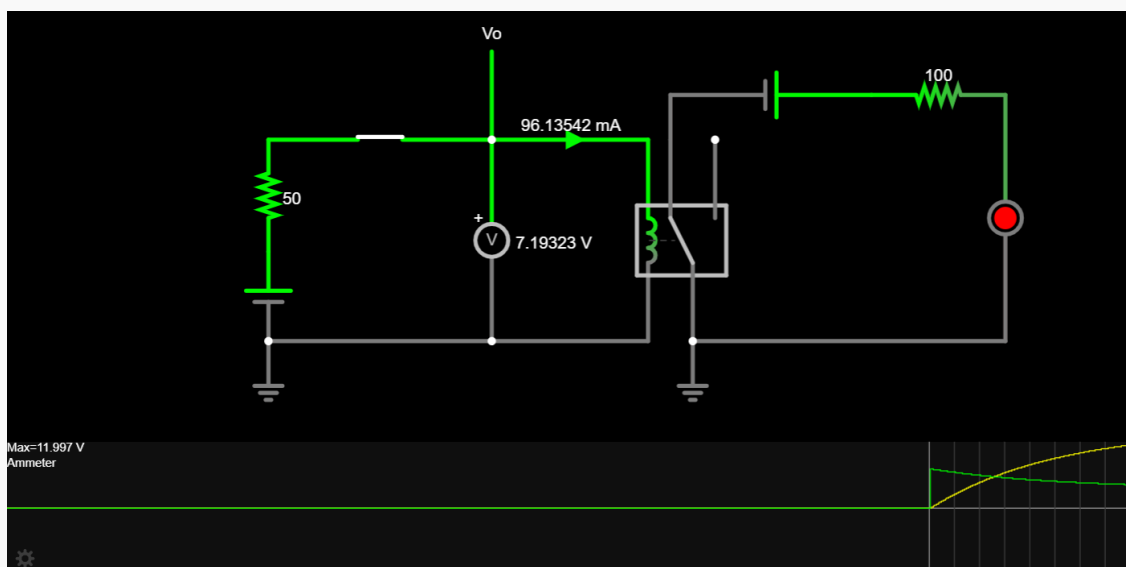4. RELAY ACTIVATION TIME

Use oscilloscopes (scopes) to measure the time it takes for the relay to activate from the time the switch is closed. That is, the time from the moment the relay is powered by the microcontroller until the LED turns on. What is the current flowing through the coil at the moment when the relay switches? Does it coincide with the data given in the previous work? NOTE: It is important to make a good selection of the time scale to take this measurement.

As expected from the previous work, the relay turns on after approximately 16.1 ms. At this moment, the current flowing through the coil is approximately 96 mA, which is exactly 80% of the stationary current (120 mA).




Falstad Link: <https://tinyurl.com/2xhwqm52>

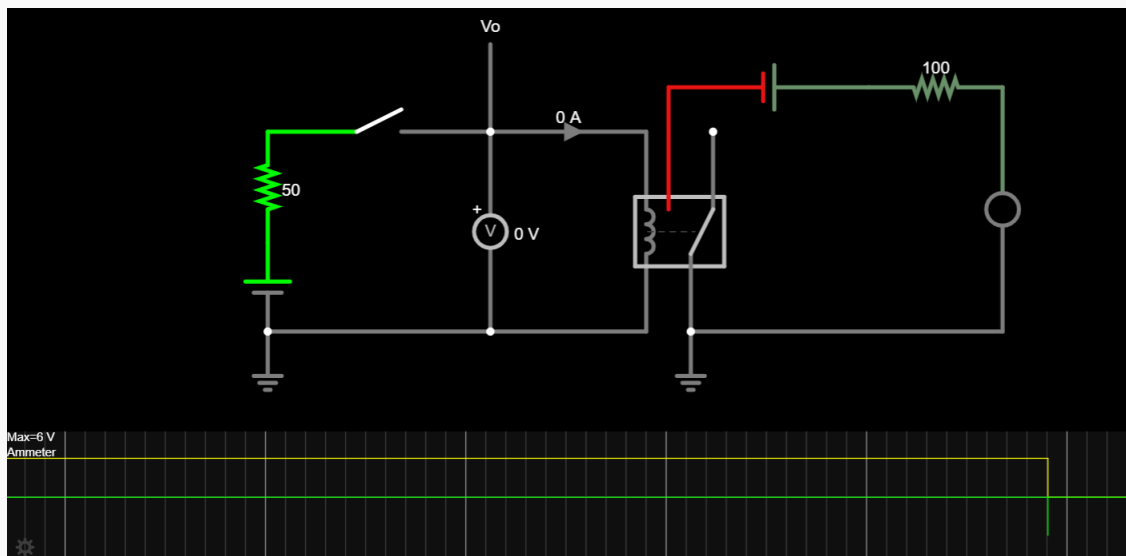5. DEACTIVATION TIME OF THE RELAY


Now we study the deactivation of the relay. Measure the time it takes for the LED to turn off (that is, for the relay to deactivate) from the moment the switch is opened. What maximum voltage in absolute value is measured at the output of the microcontroller? Explain what you observed.

The relay was switched off after a very long time, in steady state. The relay turned off immediately, as shown in the previous work. As shown in the scope graph, the current fall is instantaneous.



Falstad Link: <https://tinyurl.com/2xny4qtl>

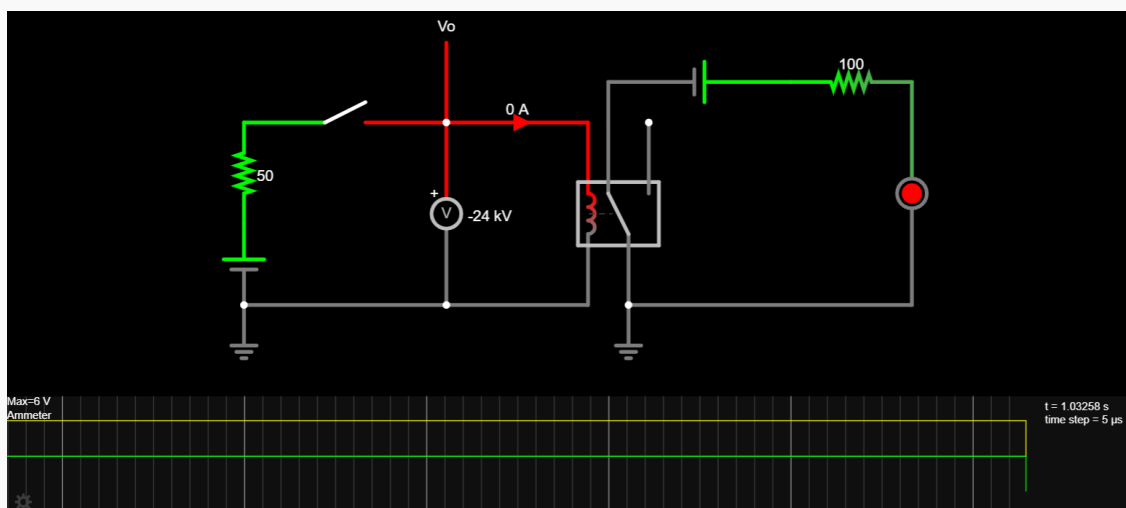As predicted in the preparatory work, there was an instantaneous unbounded voltage spike in the opposite direction. Here is a measurement of the maximum absolute value of the voltage at the output of the microcontroller. The voltmeter reported a magnitude of 24 kV, an alarmingly high value for the microcontroller.



6. EFFECT OF THE CAPACITOR IN THE DEACTIVATION OF THE RELAY


Now place the capacitor $C_p=200\text{ }\mu\text{F}$ in parallel with the relay coil. When the relay is turned off:

- What is now the maximum absolute value of voltage at the output of the microcontroller?
- How long does it now take for the relay to deactivate from the time the switch is opened (i.e., how long does it take for the LED to turn off)?
- What would happen if the relay only activated once more than 1% of the current flowed through it instead of 80%?

The maximum absolute value measured at the output of the microcontroller was now -4.087 V , a much more manageable value for the microcontroller.

The relay was deactivated after 300.1 ms , at which point the current flowing through the coil was a stable 120 mA . The relay took approximately 24 ms to deactivate, a much longer time than before, but the microcontroller was saved from the high voltage spike.

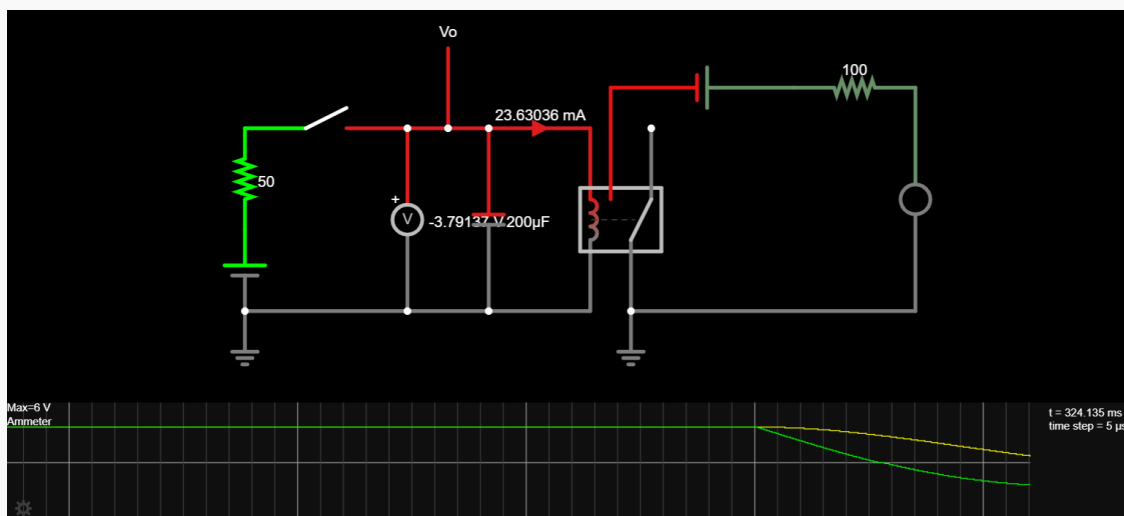If the relay could be activated with only 1% of the current flowing through it, it would also take longer to deactivate. However, adding the capacitor would be less of a problem during activation.



Falstad Link: <https://tinyurl.com/24trle45>


7. EFFECT OF THE CAPACITOR ON RELAY ACTIVATION

After placing the capacitor C_p , has the relay activation process also been affected?

What is the time it now takes for the relay to energize?

The activation process has been affected as well. The voltage at the output rises slowly with a slight oscillation, and the current rises more slowly.

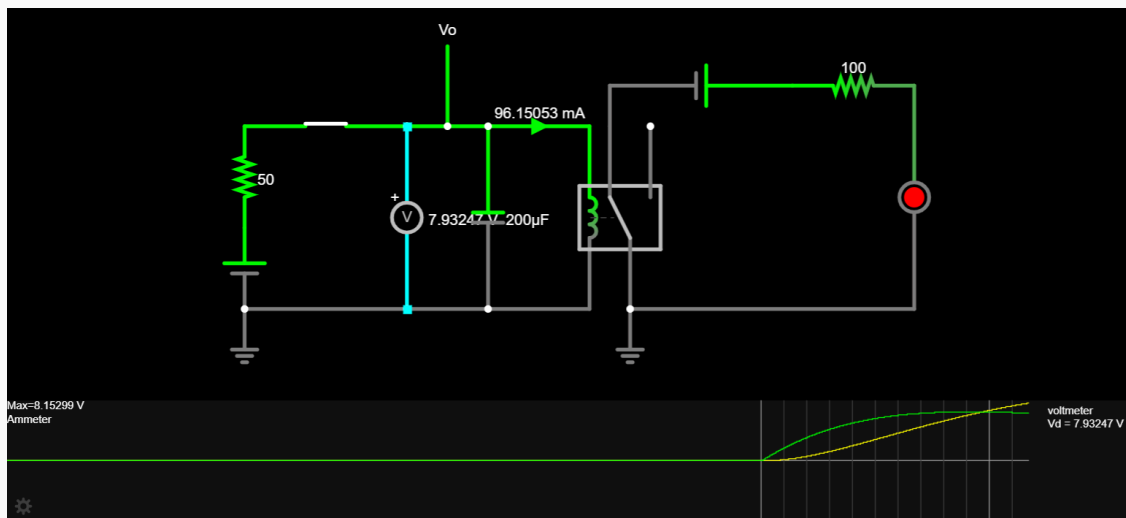The relay activation takes longer now, approximately 23.4 ms , about 45% longer than before. This is expected, as the capacitor must be charged before the current is stable.




Falstad Link: <https://tinyurl.com/259nenl9>

8. EFFECT OF CAPACITOR CAPACITY ON RELAY ACTIVATION/DEACTIVATION


Investigate and justify (especially in the relay deactivation process) what happens when instead of choosing a value of $200\ \mu\text{F}$ for the capacitor C_p the following values are chosen:

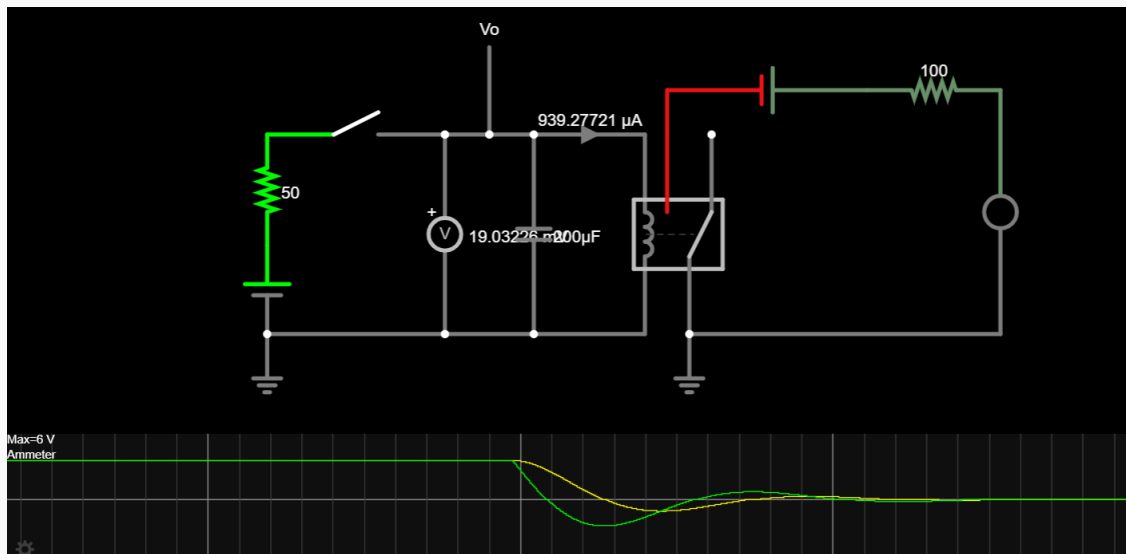1. $20\ \mu\text{F}$
2. $800\ \mu\text{F}$

At $200\ \mu\text{F}$, the relay deactivation process slow and slightly oscillating




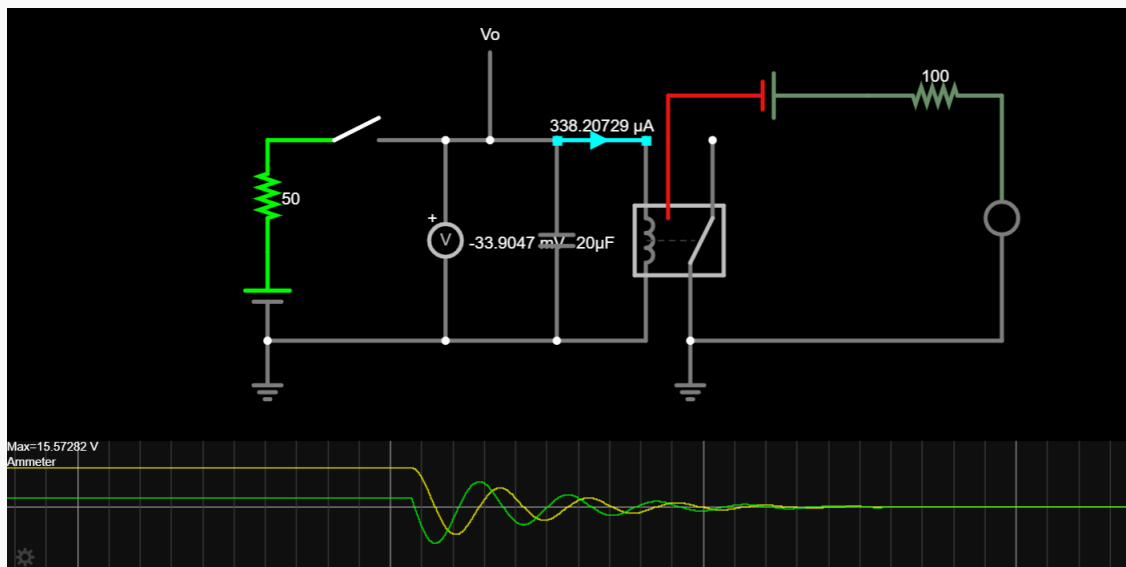At $20\ \mu\text{F}$, the relay deactivation is much faster, taking only $6.6\ \text{ms}$, but the oscillations are more pronounced. Values even lower could make the relay activate again after deactivation, if the current oscillations are too high.



Falstad Link: <https://tinyurl.com/29uv8n5u>

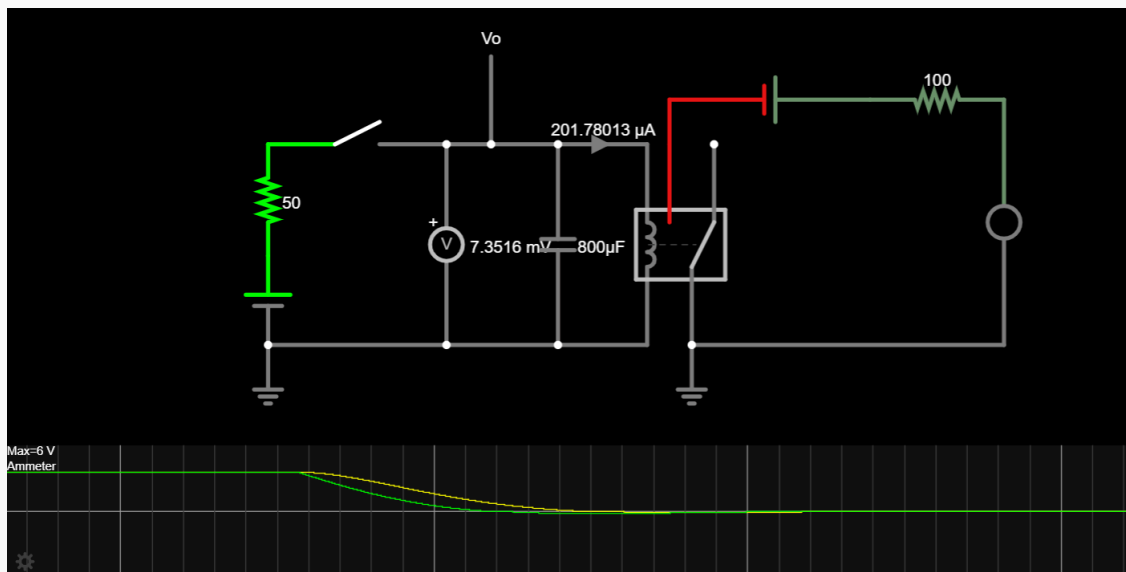At 800 µF, the relay deactivation is much slower, taking approximately 65.4 ms, but there is almost no oscillation.




Falstad Link: <https://tinyurl.com/25xa6r7h>

9. ALTERNATIVES

There are other better solutions to discharge in a controlled way the relay coil. Explore with the simulator the following alternatives:

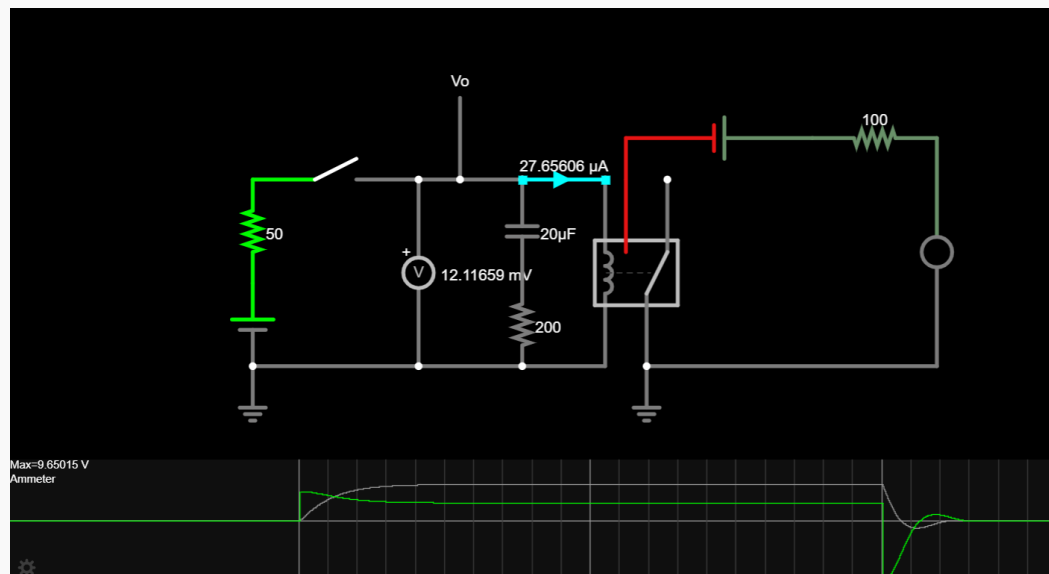1. Add a resistor in series with the capacitor C_p .


By adding a resistor with the correct value, the relay deactivation process becomes much more damped. This was tested using the 20 µF capacitor, and the relay deactivation took approximately 5.1 ms without the oscillations seen in the previous question.



Falstad Link: <https://tinyurl.com/28zz3usv>

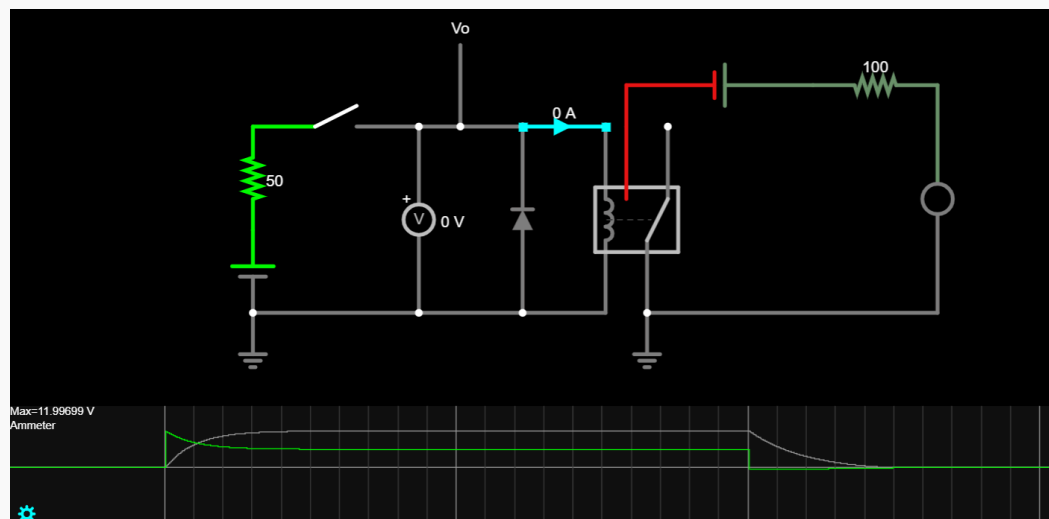2. Replace the capacitor with a diode. The diode is a nonlinear element, but its behavior can be linearized modeling the diode as a short when forward biased, and as an open when reverse biased.

By replacing the capacitor with a diode, the reverse voltage spike is eliminated, and the microcontroller is protected. The diode doesn't receive much current, but it could be protected with a resistor in series if necessary. The deactivation process was slower though, and it took approximately 26 ms.



Falstad Link: <https://tinyurl.com/2dfmnr7t>